




समस्त बिहार, भरेगा हुंकार

HUNKAR 2025

में आपका स्वागत है


⊗ Series: capacitors

→ Q Charge. sa.

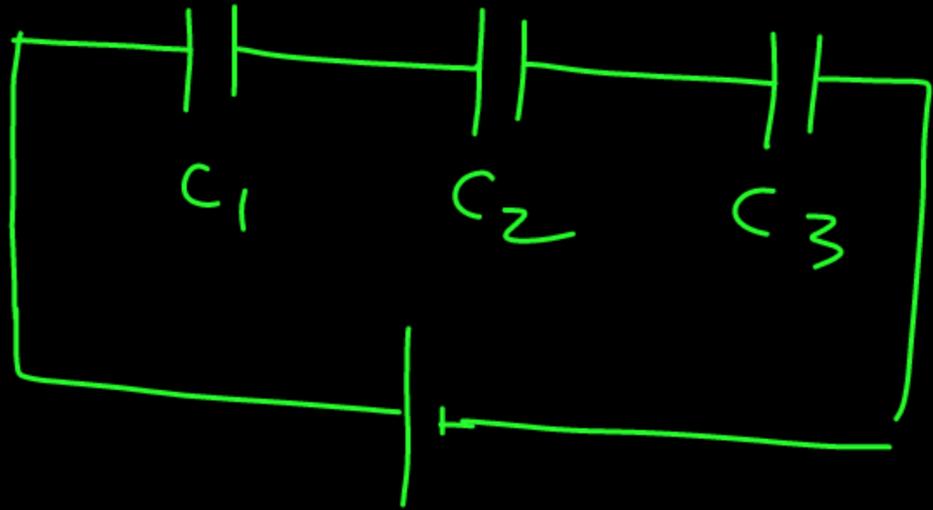

$$\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

⊗ Parallel
P. J Sam.

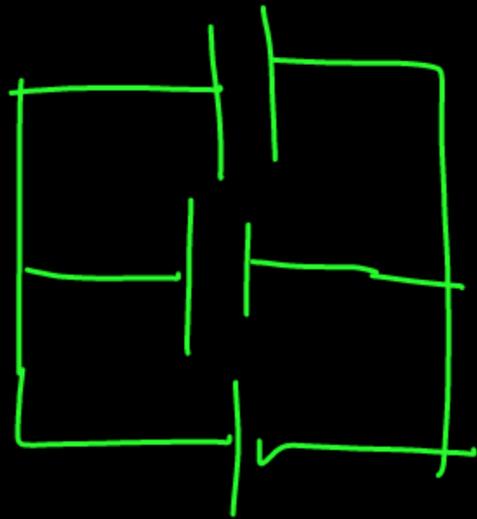


$$C_e = C_1 + C_2 + C_3$$

Resistor


⊗

current same.

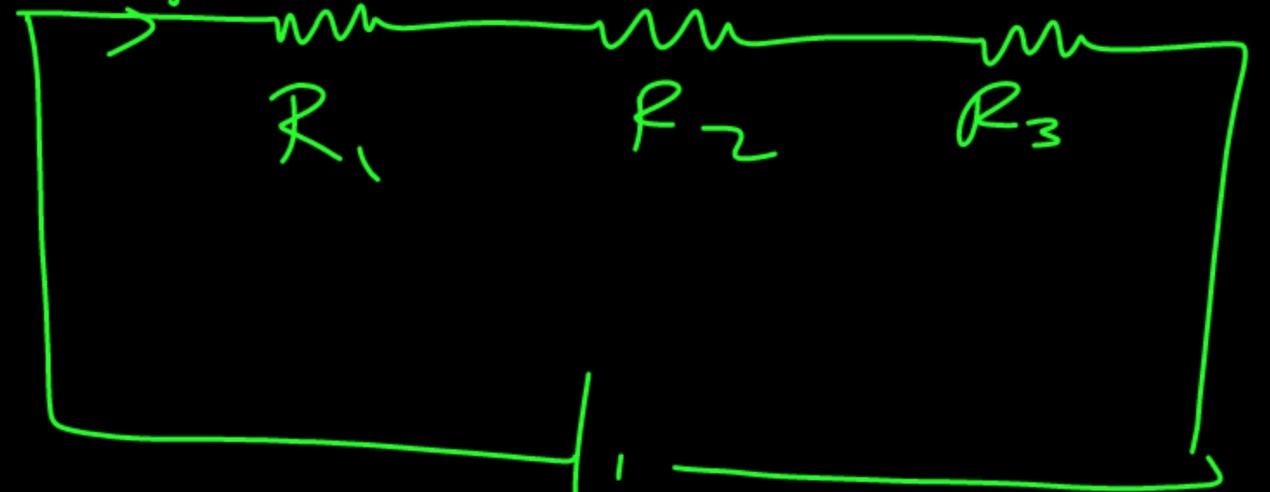

$$R_{eq} = R_1 + R_2 + R_3$$

⊗

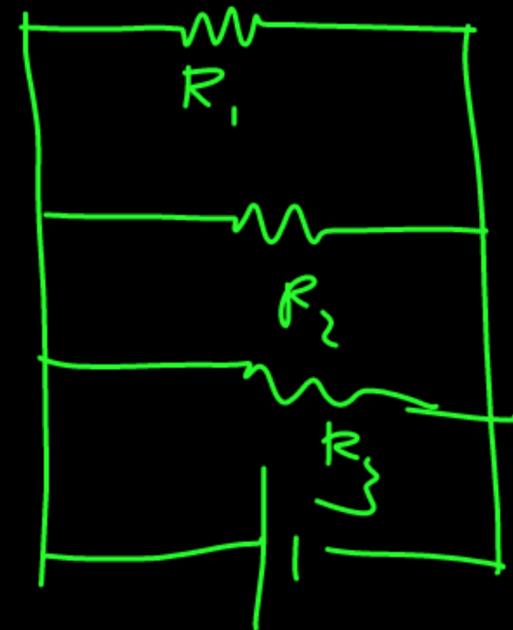

P. J Sam

$$\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

HUNKAR 2025



VIDYAKUL



PHYSICS

JP UJALA Sir

अध्याय 03


Wheat Stone Bridge

& Combination of Resistors.
प्रतिरोधकों का समूह


आज का टॉपिक

⊛ Problems based on combination of resistor.
प्रतिरोधकों के समूह पर आधारित प्रश्न.


i)

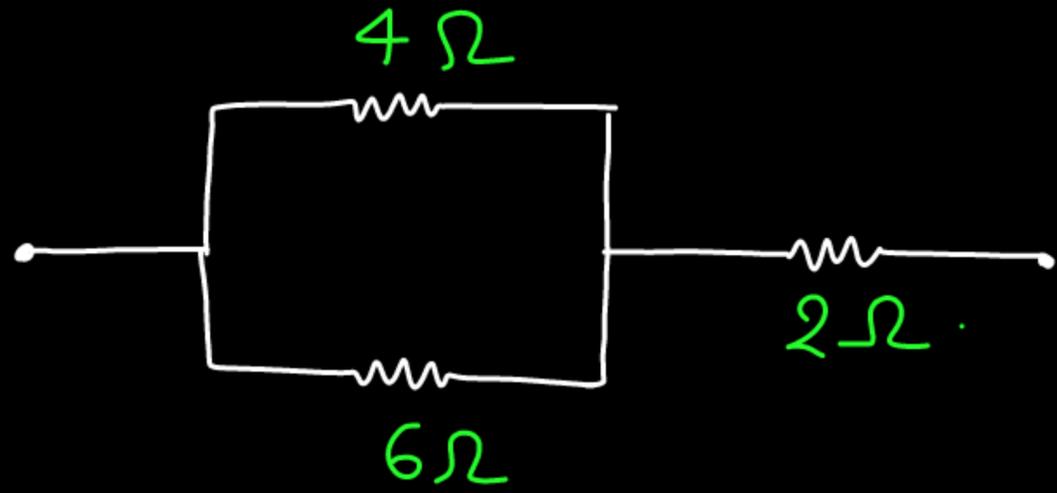


(ii)

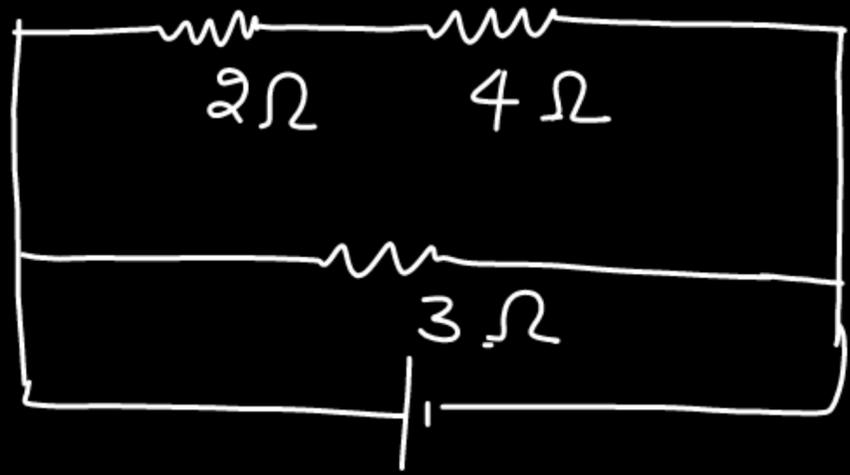


(iii)

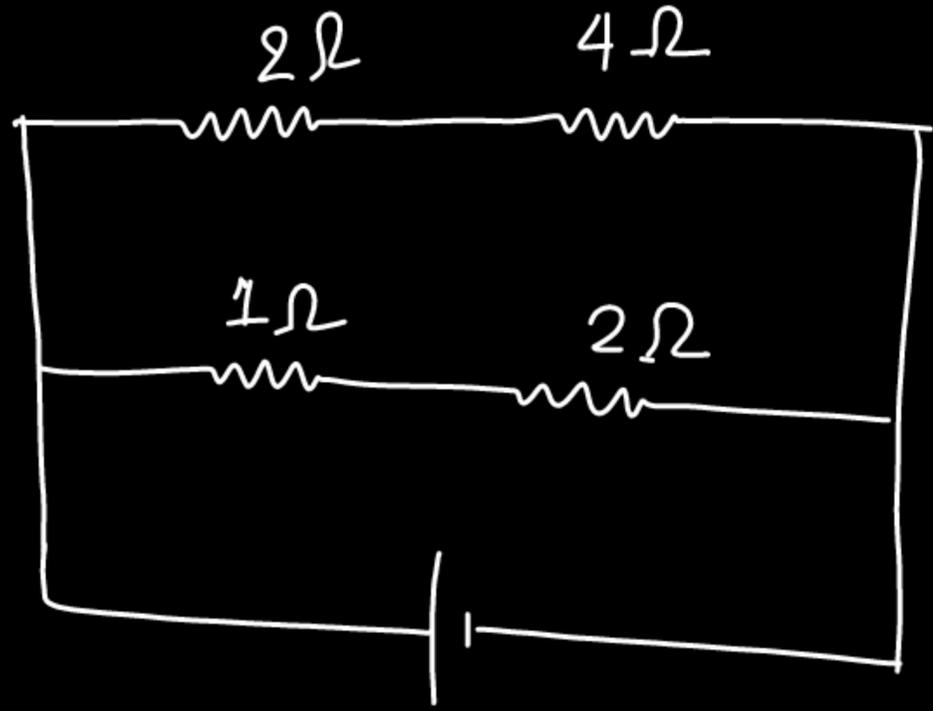


iv)

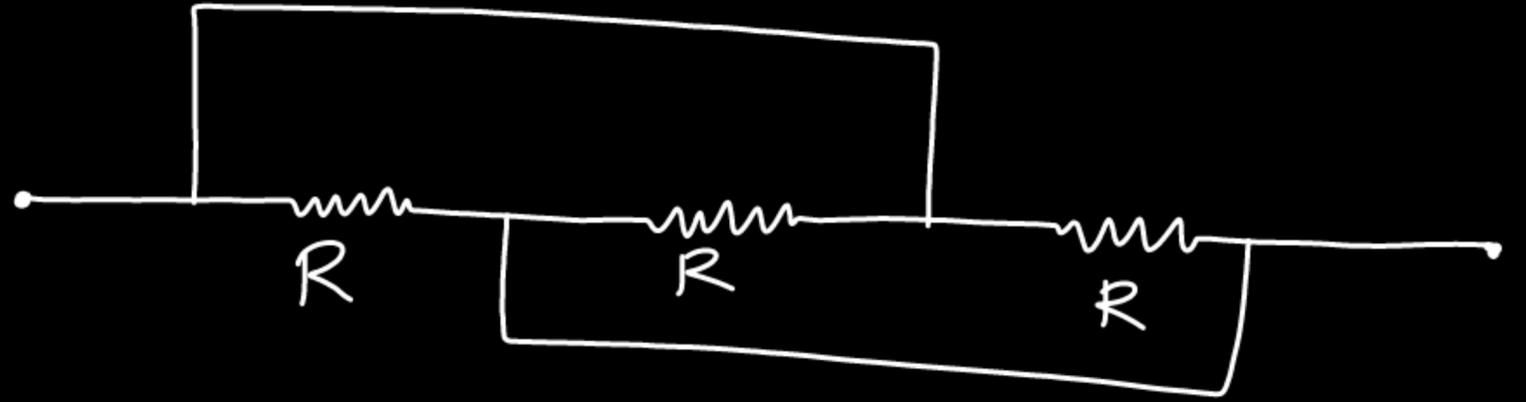

v)

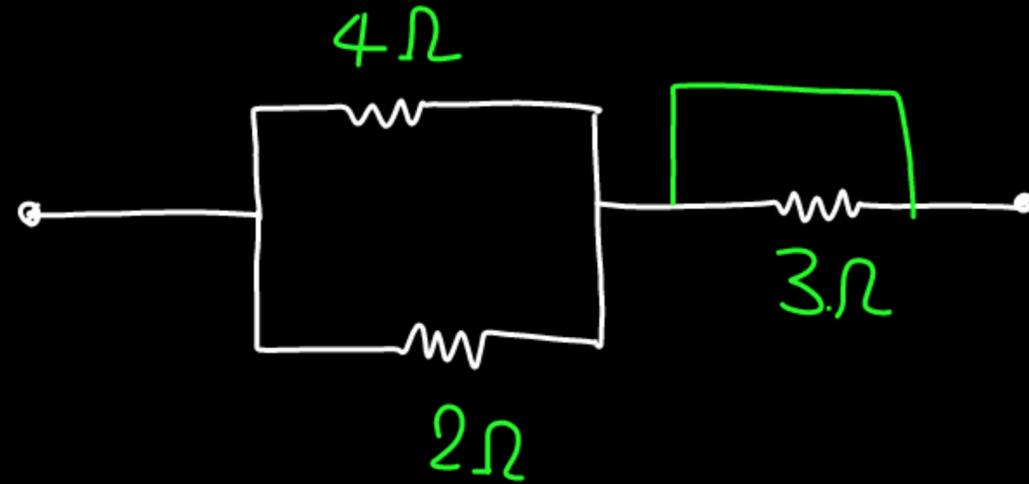

(VI)

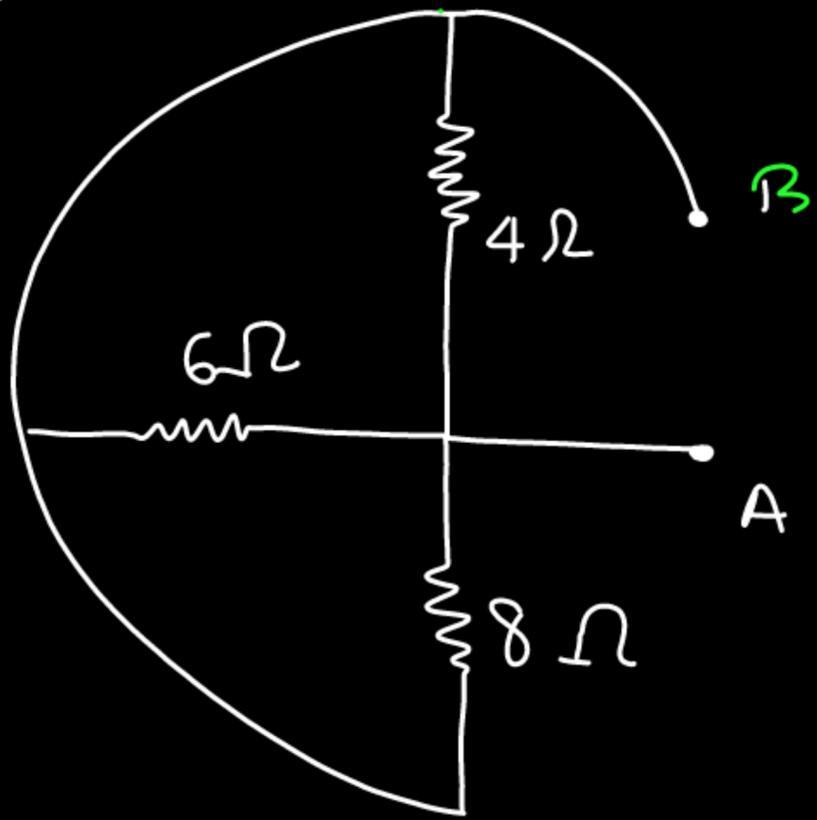

WHEATSTONE BRIDGE

It is an arrangement of four resistors used for measuring resistance of one of them in terms of other three. It was devised by sir Charles wheatstone a British physicist in 1833.

In this circuit there are four resistors connected as shown in circuit there is a bridge element connected between them which is a galvanometer.

There are two types of wheatstone bridge.

1. Balanced wheatstone bridge
2. Unbalanced wheatstone bridge


यह चार प्रतिरोधकों का ऐसा संयोजन है जिस के उपयोग से इनमें से एक प्रतिरोधक का प्रतिरोध बाकी तीन प्रतिरोधकों के प्रतिरोध के पद में ज्ञात कर सकते हैं।

इस परिपथ में चार प्रतिरोधक जुड़े रहते हैं तथा इनके बीच एक सेतु अवयव जुड़ा रहता है जो एक गैल्वेनोमीटर होता है।

यह दो प्रकार का होता है।

WHEATSTONE BRIDGE

WHEATSTONE BRIDGE

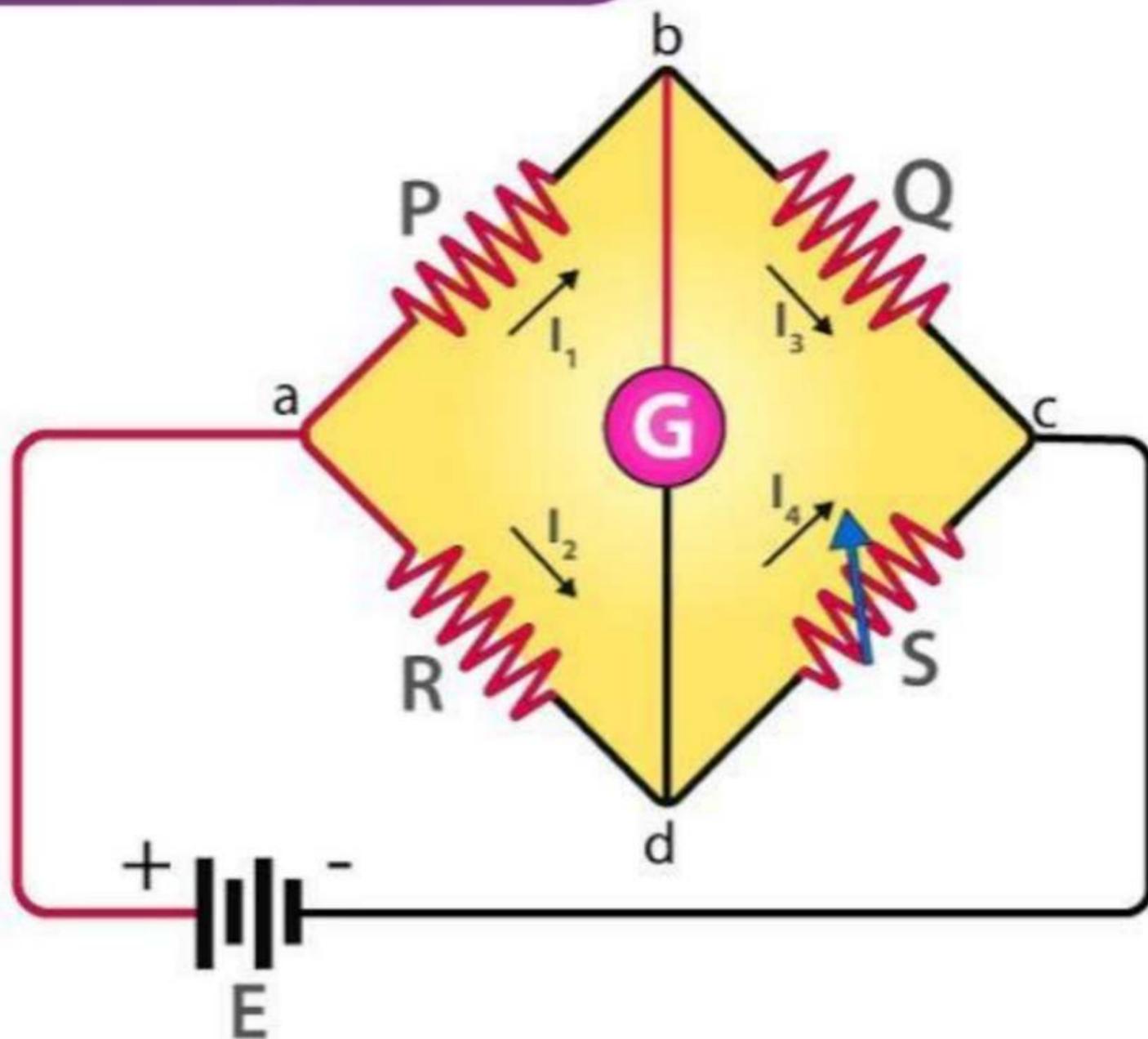

BALANCED WHEATSTONE BRIDGE

संतुलित व्हीटस्टोन ब्रिज


The wheatstone bridge in which there is no current passes from bridge element is called balanced wheatstone bridge.

ऐसा व्हीटस्टोन ब्रिज जिसमें सेतु अवयव से कोई धारा नहीं गुजरती हो उसे संतुलित व्हीटस्टोन ब्रिज कहते हैं।

Condition for balanced wheatstone bridge.

संतुलित व्हीटस्टोन ब्रिज का शर्त

⊛ Proof

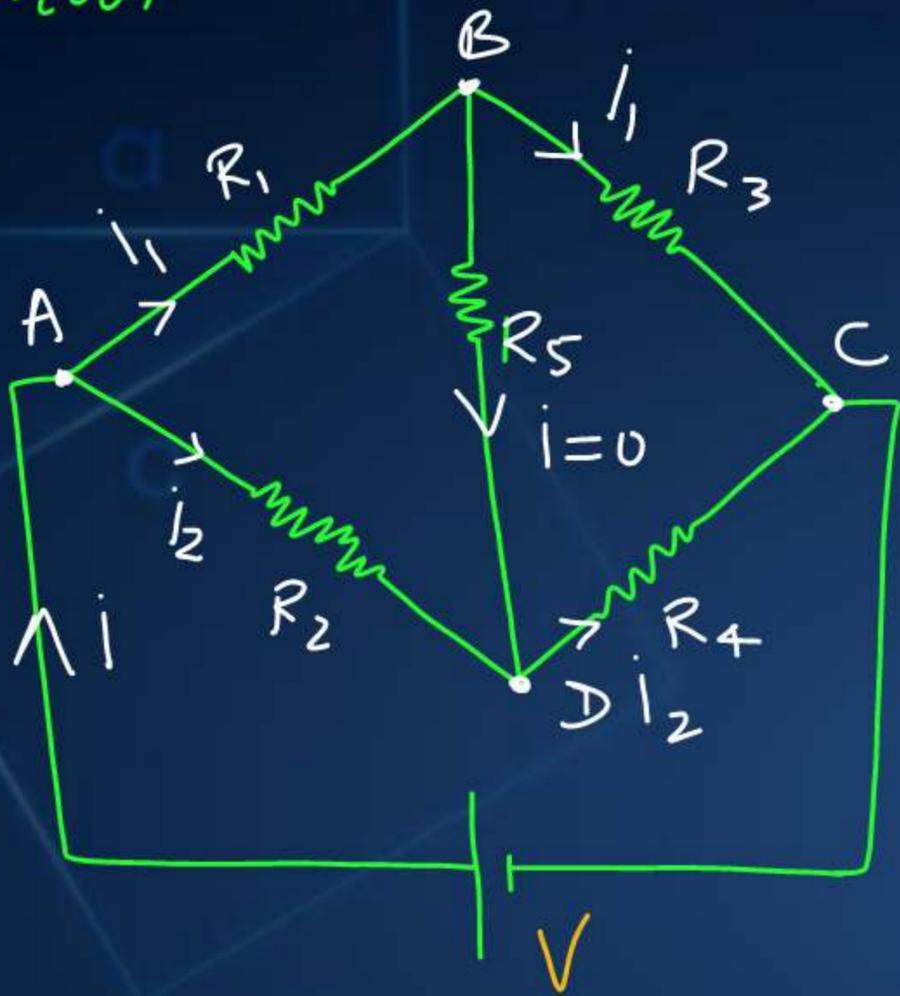

$$V_A - V_B = i_1 R_1 \quad \text{--- (i)}$$

$$V_B - V_C = i_1 R_3 \quad \text{--- (ii)}$$

$$\frac{V_A - V_B}{V_B - V_C} = \frac{R_1}{R_3} \quad \text{--- (V)}$$

Divide

$$V_A - V_D = i_2 R_2 \quad \text{--- (iii)}$$

$$V_D - V_C = i_2 R_4 \quad \text{--- (iv)}$$

$$\frac{V_A - V_D}{V_D - V_C} = \frac{R_2}{R_4} \quad \text{--- (vi)}$$

चुकि R5 लैधारा शून्य है शक्ति
 Since current through R5 is zero so

$$V_B = V_D$$

Putting V_B on the place of V_D in eqn (vi)

$$\frac{V_A - V_B}{V_B - V_C} = \frac{R_2}{R_4} \quad \text{--- (vii)}$$

From eqn (V) & (VII)



$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$



Proved



$$V_A - V_B = iR$$

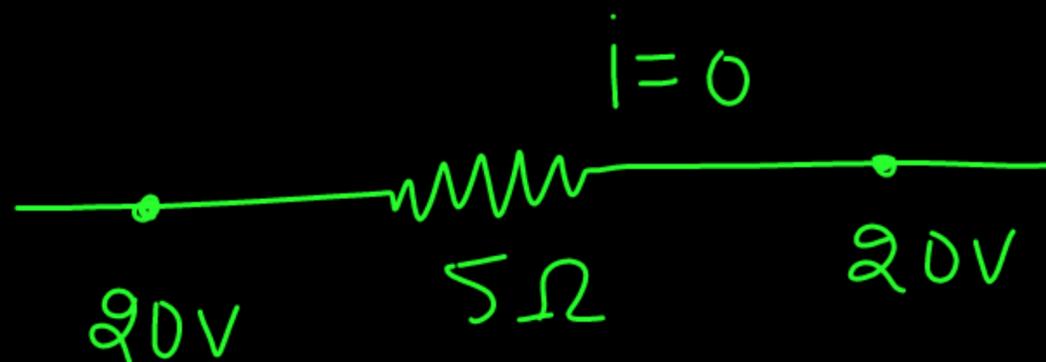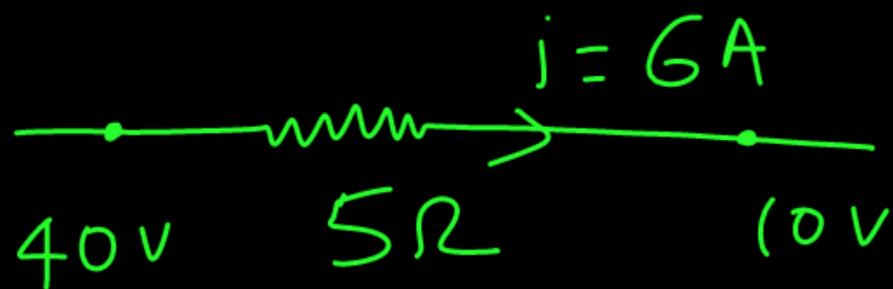

(*)

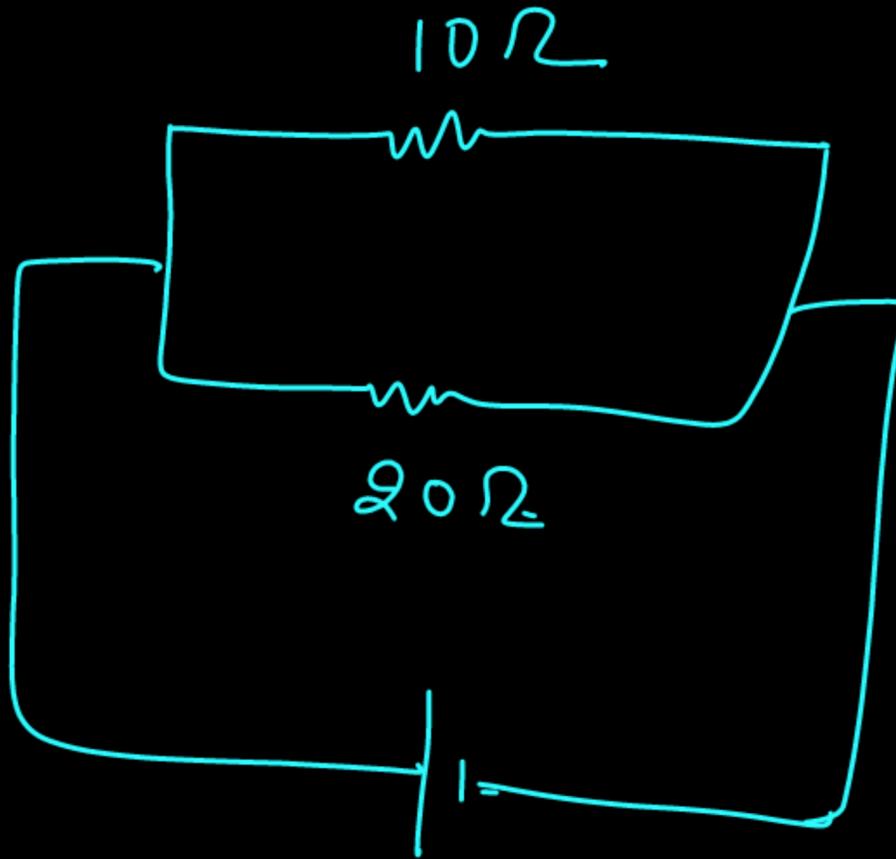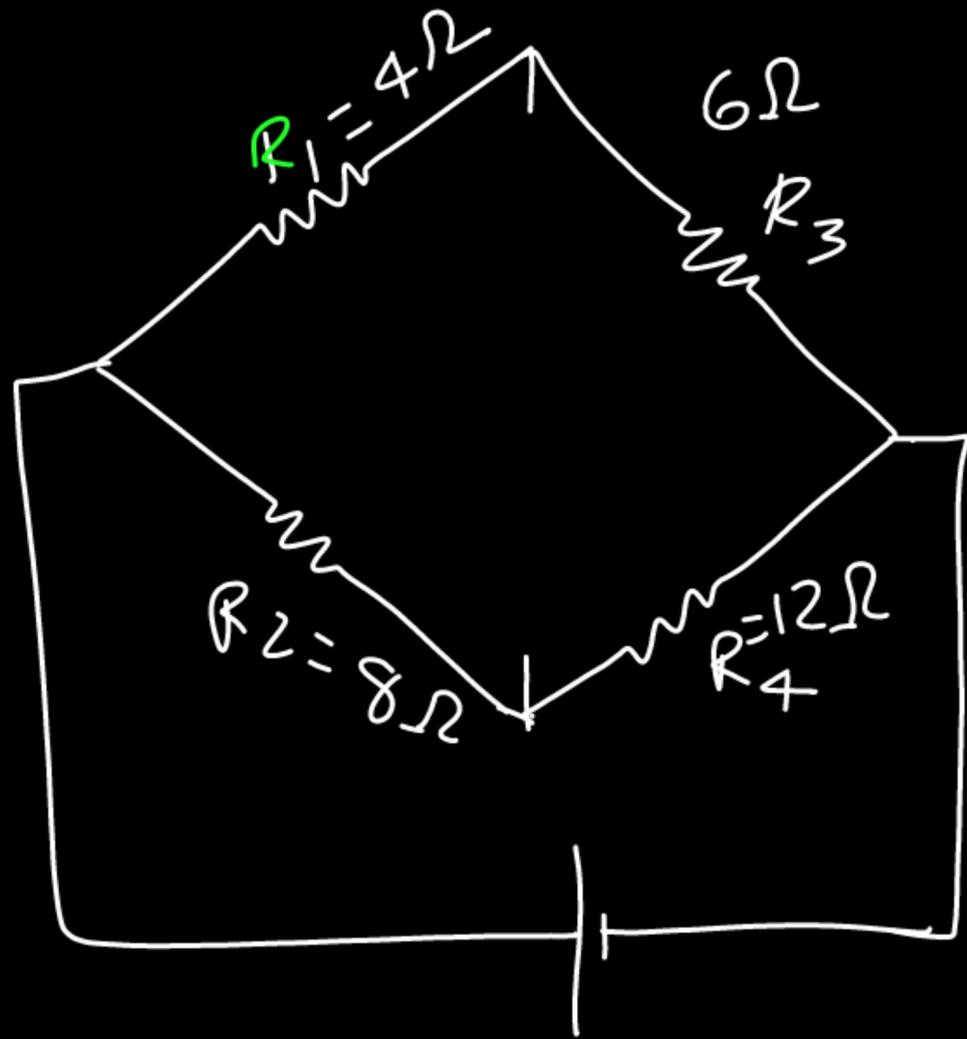

$$\frac{1}{R_e} = \frac{1}{10} + \frac{1}{20}$$

$$\frac{1}{R_e} = \frac{2+1}{20}$$

$$R_e = \frac{20}{3} \Omega$$

* HW Find the Req.

